

Al-Saudia Virtual Academy

www.pakistanonlinetuition.com

www.onlinetutorpakistan.com

Electrical Measuring Instruments

Chapter No.15 (MCQs)

- A galvanometer is an electromechanical device, it converts:
 - Mechanical energy into electrical energy.
 - Electrical energy into mechanical energy.
 - Elastic energy into electrical energy.
 - Electromagnetic energy into mechanical energy.
- Principle of working of a galvanometer is that:
 - A current carrying coil experiences attractive force in a magnetic field.
 - A current carrying coil experiences repulsive force in a magnetic field.
 - A current carrying coil experiences torque in a magnetic field.
 - None of these.
- In a moving coil galvanometer poles of the magnet are made concave shaped due to which:
 - Magnetic field is strong and uniform.
 - Magnetic field is strong and radial.
 - Magnetic field is weak and uniform.
 - Magnetic field is weak and radial.
- For a radial magnetic field the angle α between the plane of coil and the magnetic field is:
 - 0°
 - 30°
 - 60°
 - 90°
- Sensitivity of a galvanometer can be increased by:
 - Increasing the number of turns and area of the coil.
 - Using a strong magnet.
 - Decreasing couple per unit twist of the suspension wire.
 - All of these.
- A galvanometer can be converted into an ammeter.
 - By connecting a low resistance in series to its coil.
 - By connecting a low resistance in parallel to its coil.
 - By connecting a high resistance in series to its coil.
 - By connecting a high resistance in parallel to its coil.
- In order to measure current with maximum accuracy. The resistance of the ammeter must be:
 - High.
 - Very high.
 - Low.
 - Very low.
- If R_g is the shunt resistance, then the resistance of an ammeter is given by:
 - $R_A = R_g + R_S$.
 - $R_A = 1/R_g + 1/R_S$
 - $1/R_A = 1/R_g + 1/R_S$
 - $1/R_A = 1/R_g - 1/R_S$.
- An ammeter is connected:
 - In parallel to the circuit.
 - In series to the circuit.
 - Sometimes in series some times in parallel to the circuit.
- Ammeter is used to measure:
 - Charge.
 - Current.
 - Potential difference.
 - Emf.
- Voltmeter is used to measure:
 - Charge.
 - Current.
 - Potential difference.
 - Resistance.
- A galvanometer can be converted into a voltmeter by connecting:
 - A low resistance in series to its coil.
 - A low resistance in parallel to its coil.
 - A high resistance in series to its coil.
 - A high resistance in parallel to its coil.

13. A voltmeter is connected:

- a) In parallel to the circuit.
- b) In series to the circuit.
- c) Some times in series some times in parallel to the circuit.

14. For accurate measurement of potential difference the resistance of the voltmeter must be:

- a) High.
- b) Very high.
- c) Low.
- d) Very low.

15. If R_g is the resistance of coil of a galvanometer, R_x is the value of series resistor, and then the resistance R_V of a voltmeter is given by:

- a) $R_V = R_g + R_x$.
- b) $R_V = 1/R_g + 1/R_x$.
- c) $1/R_V = 1/R_g + 1/R_x$.
- d) $1/R_V = 1/R_g - 1/R_x$.

16. The value of shunt resistance R_s required converting a galvanometer of resistance R_g into an ammeter of range "I" can be calculated by:

- a) $R_s = I_g R_g / (I - I_g)$
- b) $1/R_s = I_g R_g / (I - I_g)$
- c) $R_s = (I - I_g) / I_g R_g$
- d) $1/R_s = (I - I_g) / I_g R_g$

17. The value of series resistance R_x required to convert a galvanometer of resistance R_g into a voltmeter of range "V" can be calculated by:

- a) $R_x = I_g R_g / (I - I_g)$
- b) $R_x = V/I_g - R_g$
- c) $R_x = V/R_g - I_g$
- d) $R_x = I_g R_g - V / (I - I_g)$

18. When a Wheatstone bridge of resistance arms R_1 , R_2 , R_3 and R_4 is balanced:

- a) No current flows through the galvanometer.
- b) No current flows through its arms.
- c) Some current flows through the galvanometer.
- d) There is no potential difference across the galvanometer.

19. Meter Bridge is based on:

- a) Circuital law.
- b) Coulomb's law.
- c) Wheatstone bridge principle.
- d) Ampere's law.

20. If the resistance of a galvanometer is 50Ω the resistance of ammeter having a 0.1Ω shunt will be:

- a) 50.1Ω .
- b) 5.01Ω .
- c) 0.501Ω .
- d) 0.01Ω .

21. If the resistance of a galvanometer is 50Ω the resistance of voltmeter having a 5000Ω series resistance will be:

- a) 5050Ω .
- b) 500.01Ω .
- c) 0.501Ω .
- d) 0.01Ω .

22. To increase the accuracy in a potentiometer circuit: (5-a, 1997, 99)

- a) A wire of small length should be used.
- b) A wire of large length should be used.
- c) A non uniform wire is used.

23. All the electrical appliances are connected in parallel to each other between the main line and the neutral wire to get:

- a) The same current.
- b) The same potential difference.
- c) Different current and the same potential difference.
- d) None of the above.

24. A galvanometer can be used to measure current by connecting:

- a) Low resistance in series.
- b) High resistance in series.
- c) Low resistance in parallel.
- d) High resistance in parallel.

25. A galvanometer can be converted into an ammeter by connecting: (6-a, 2002, P.E)

- a) Low resistance in series.
- b) High resistance in series.
- c) Low resistance in parallel.
- d) High resistance in parallel.

26. Potentiometer is a device for measuring: (4-a, 2003 PM)

- a) Potential difference between the two points of a circuit. (4-a, 2003 PM)
- b) Voltage between the two points of a circuit.
- c) E.M.F of a current source.
- d) All of them.

27. Total potential difference across the combination of three cells becomes maximum when (4-a, 2003 PM)

- a) All of the three cells are connected in series.
- b) All of the three cells are connected in parallel.
- c) Two cells are connected in parallel and the third cell in series with the combination.
- d) Two cells are connected in series and the third cell in parallel with the combination.

28. A meter bridge is used to measure: (6-a, 2002, P.E)

- a) Voltage.
- b) Inductance.
- c) Capacitance.
- d) Resistance.

29. AVO meter is used to measure: (5-a, 2002, P.E)

- a) Current.
- b) Voltage.
- c) Resistance.
- d) All of them.

30. A single device containing ammeter, voltmeter and ohmmeter is called: (1-vi, 2010)

- a) VTVM.
- b) CRO.
- c) Potentiometer.
- d) Multi-meter.

ANSWERS

- (1) Electrical energy into mechanical energy.
- (2) A current carrying coil experiences torque in a magnetic field.
- (3) Magnetic field is strong and radial.
- (4) 0° .
- (5) All of these.
- (6) By connecting a low resistance in parallel to its coil.
- (7) Very low.
- (8) $1/R_A = 1/R_g + 1/R_s$.
- (9) In series to the circuit.
- (10) Current.
- (11) Potential difference.
- (12) A high resistance in series to its coil.
- (13) In parallel to the circuit.
- (14) Very high.
- (15) $R_V = R_g + R_x$.
- (16) $R_s = I_g R_g / (I - I_g)$
- (17) $R_x = V/I_g - R_g$.
- (18) No current flows through the galvanometer.
- (19) Wheatstone bridge principle.
- (20) 0.01Ω .
- (21) 5050Ω .
- (22) A wire of large length should be used.
- (23) Different current and the same potential difference.
- (24) Low resistance in parallel.
- (25) Low resistance in parallel.
- (26) All of them.
- (27) All of the three cells are connected in series.
- (28) Resistance.
- (29) All of them.
- (30) Multi-meter.

AL-Saudia Virtual Academy